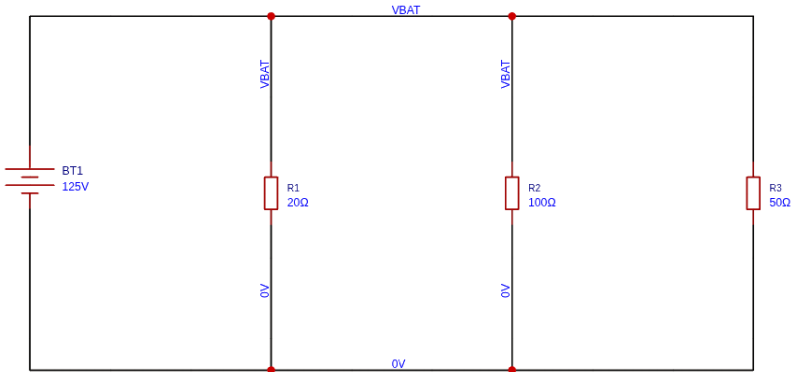


Part B (1) - Schematic for Circuit (b): Parallel resistor circuit

Circuit (b): 125 V supply with 20 Ω , 100 Ω and 50 Ω resistors in PARALLEL



$R_{total} = 12.5 \Omega$, $I_{total} = 10 A$

Schematic	circuit_e_b_parallel		Create at	2026-10-05
			Update at	2026-10-05
Board			Page	P1
Drawn		Circuit-Design		
Reviewed				
		Version	Size	Page 1 Total 1
EasyEDA		V1.0	A4	EasyEDA.com